



Highest Performance
Efficiency

POWERMATER
SEMICONDUCTOR




Masters of Power Solution

eSiC MOSFET Selection Guide 2022


Advanced Power Master Semiconductor's Silicon Carbide Technology

www.powermastersemi.com

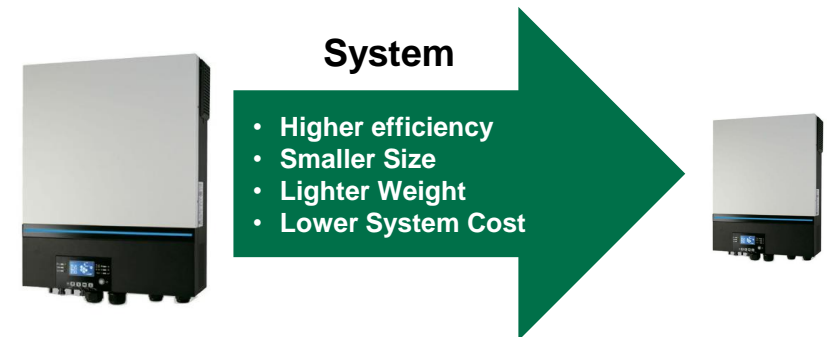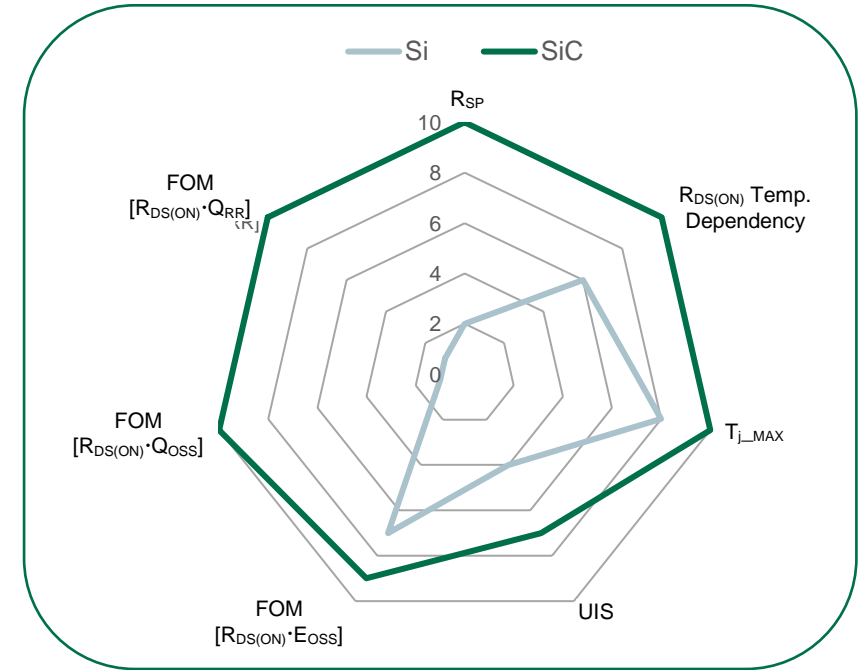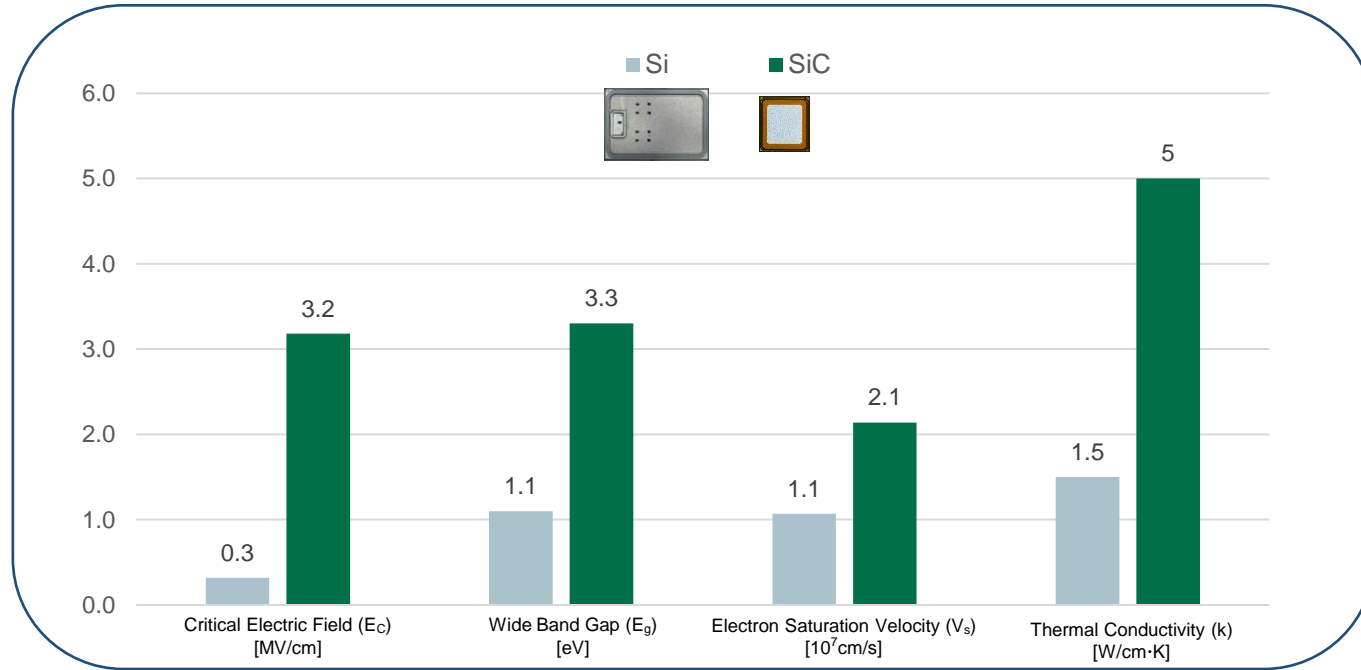Advantages of Silicon Carbide (SiC) as a Power Devices




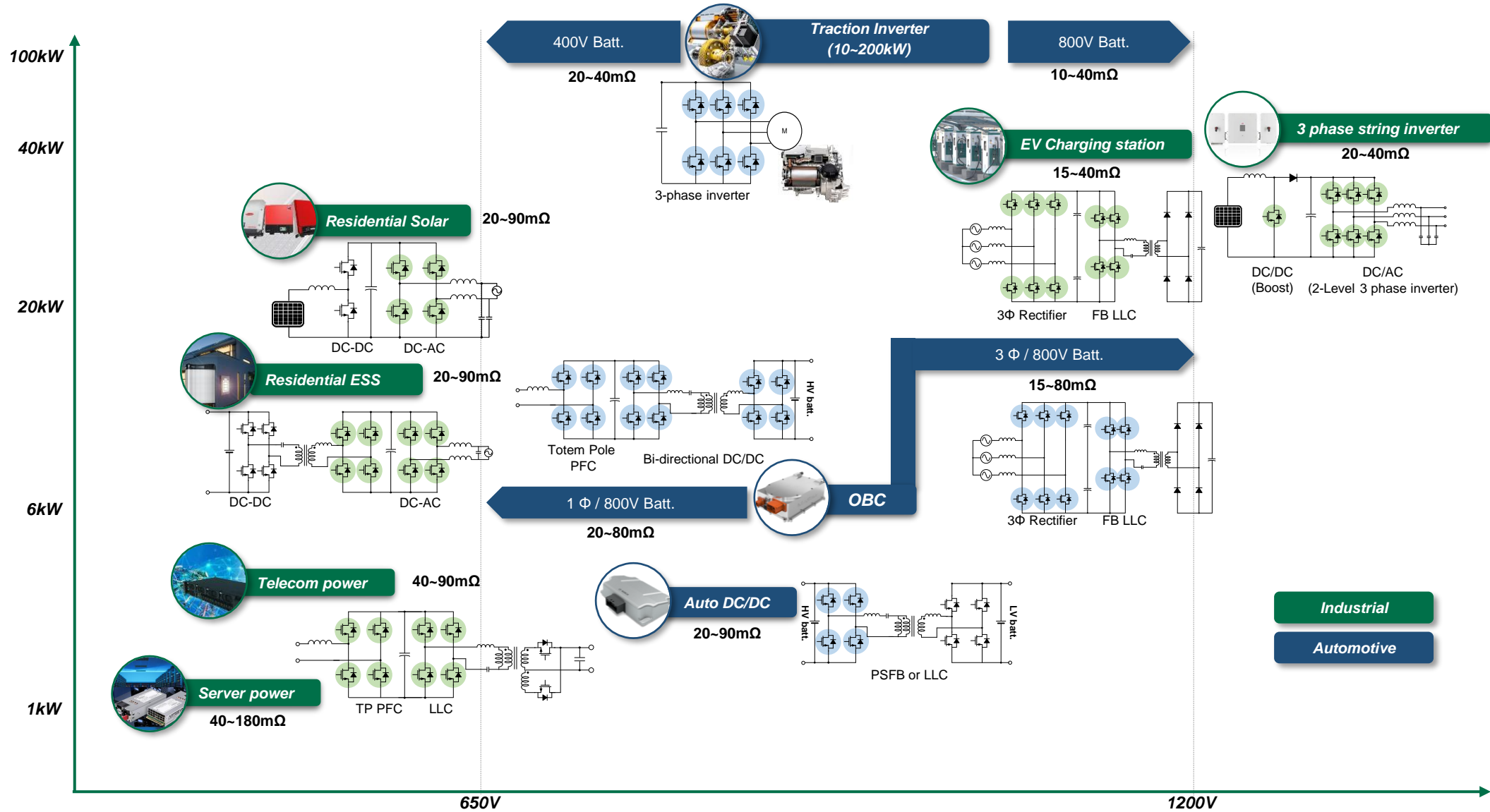eSiC MOSFET's Target Applications & Topologies




Industrial
Automotive

eSiC MOSFET Product Portfolio

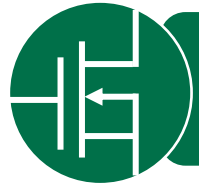

1200V SiC MOSFET

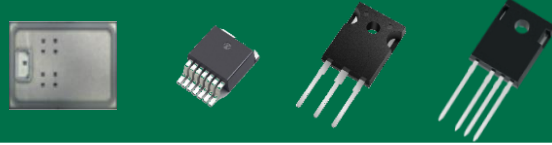

21 / 30 / 40 / 60 / 80mΩ
Die : 5 Parts / Package : 15 Parts



xEV



Solar Inverter




EV Charging Pole




UPS



Industrial Motors

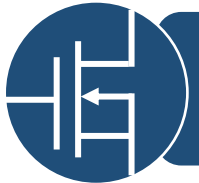

650V SiC MOSFET

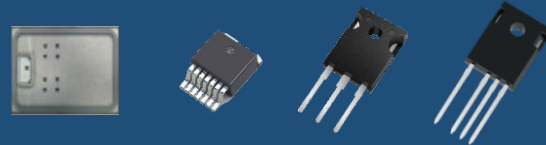

18 / 27 / 48 / 72 / 107mΩ
Die : 5 Parts / Package : 15 Parts



TV&LED lighting



xEV




Telecom/Server (w. UPS)



Solar Inverter



EV Charging Pole

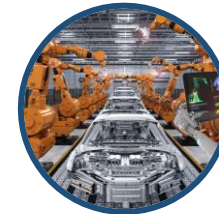

Industrial Motors

Product Differentiation

High Efficiency
(for Non-motor control)

High Ruggedness (SCWT)
(for Motor control)


1200V *e*SiC MOSFET - Features & Benefits

Power Master Semiconductor's advanced *e*SiC MOSFET provides design flexibility for high system efficiency, higher switching frequency for system size reduction with higher reliability thanks to its extremely low switching losses, low FOM [$Q_G \times R_{DS(on)}$], no reverse recovery losses of body diode and high ruggedness.

Features

- Extremely low switching losses
- Low FOM ; $Q_G \times R_{DS(on)}$
- Fast intrinsic diode
- Robust Avalanche Capability

Performance Benchmark

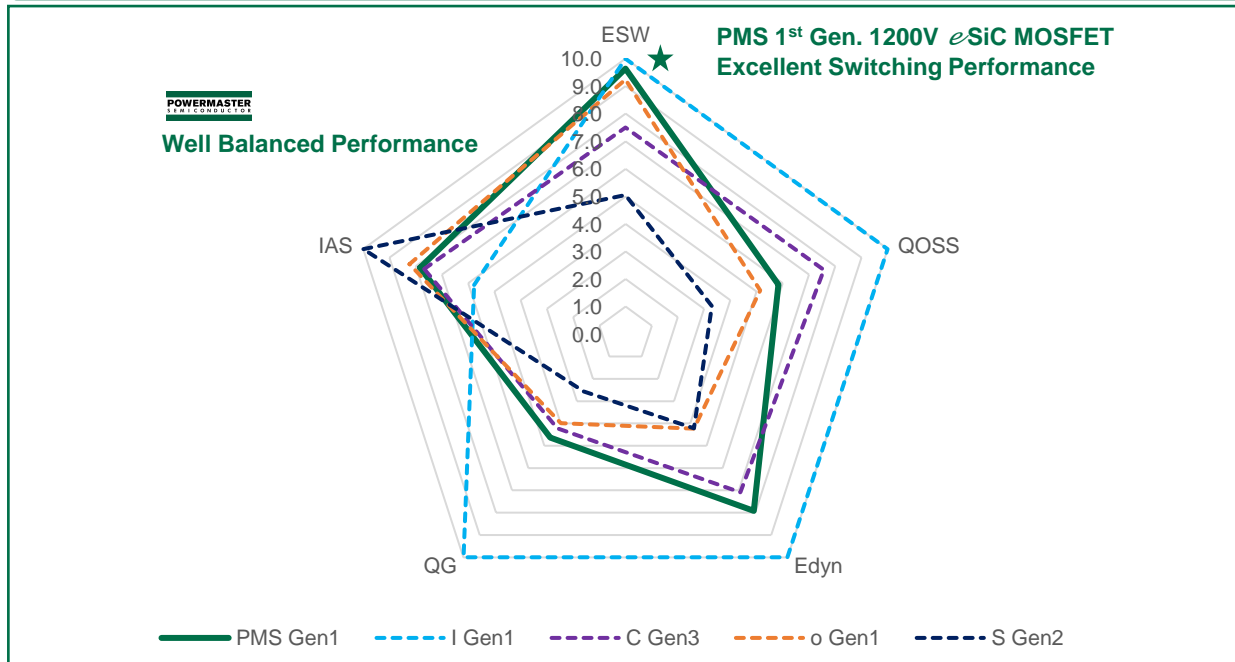

System Benefits

- Higher system efficiency
- Higher frequency applicability
- Increased power density
- Higher system reliability
- Reduced cooling effort


Target Applications



1200V / 40mΩ *e*SiC MOSFET - Switching Performance

PCW120N40M1 vs. Competitors


PMS *e*SiC MOSFET shows well balanced performance against major Players

$I_D=40A$	Best ←  → Worst					
Eon [uJ]	PMS / Comp. C PCW120N40M1 943	Comp. S 947	Comp. I 950	Comp. O 1073	Comp. R 1267	
Eoff [uJ]	PMS PCW120N40M1 203	Comp. C 207	Comp. I 238	Comp. O 244	Comp. S SCTW60N120G2 314	Comp. R 513
Total SW Losses [uJ]	PMS PCW120N40M1 1147	Comp. C 1150	Comp. I 1188	Comp. S 1261	Comp. O 1317	Comp. R 1780
Peak Vds [V]	Comp. R 1008	PMS / Comp. C / Comp. O PCW120N40M1 1024			Comp. S 1027	Comp. I 1028
Negative Vgs [V]	PMS PCW120N40M1 - 5.8	Comp. I / Comp. O - 6.4		Comp. C - 6.6	Comp. R - 6.8	Comp. S - 8.0

1200V / 40mΩ *e*SiC MOSFET Switching Losses

PCW120N40M1 vs. Competitors

Excellent switching performance


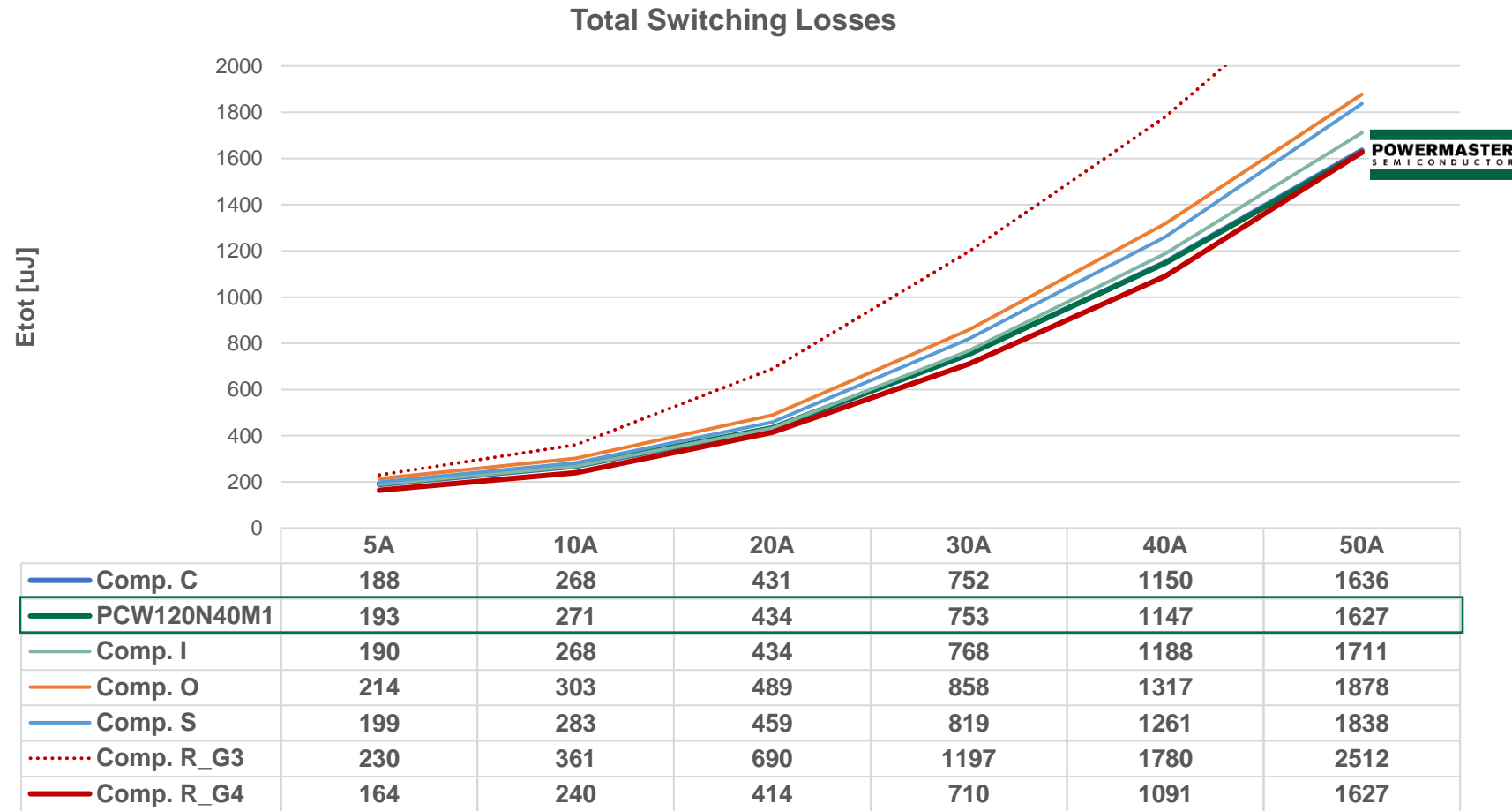


- Note
- * $V_{DD}=800V$, $R_G=2\Omega$, $V_{GS}=-3V\sim 18V$, $I_D=10A, 20A$, FWD=PCH120S10D1(1200V/10A)

1200V / 40mΩ *e*SiC MOSFET Switching Noise



PCW120N40M1 vs. Competitors

Lower Switching Noise

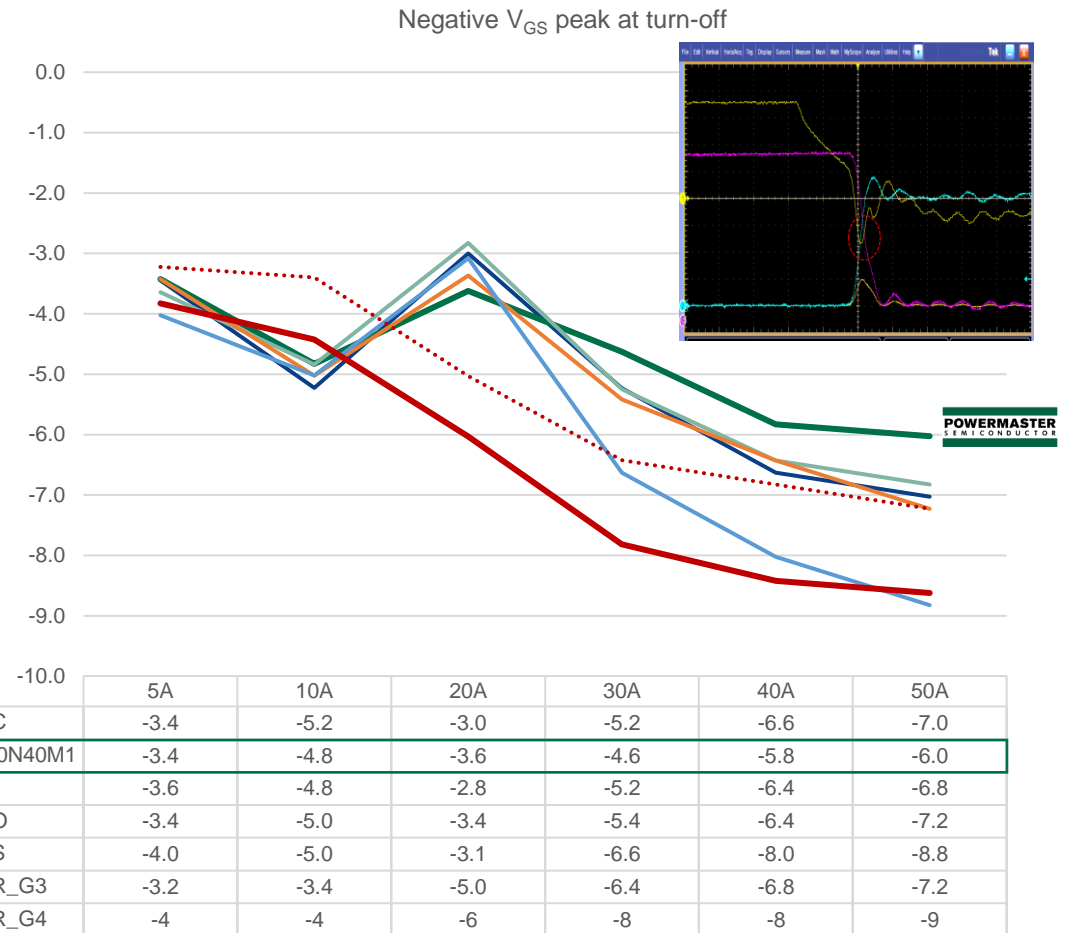
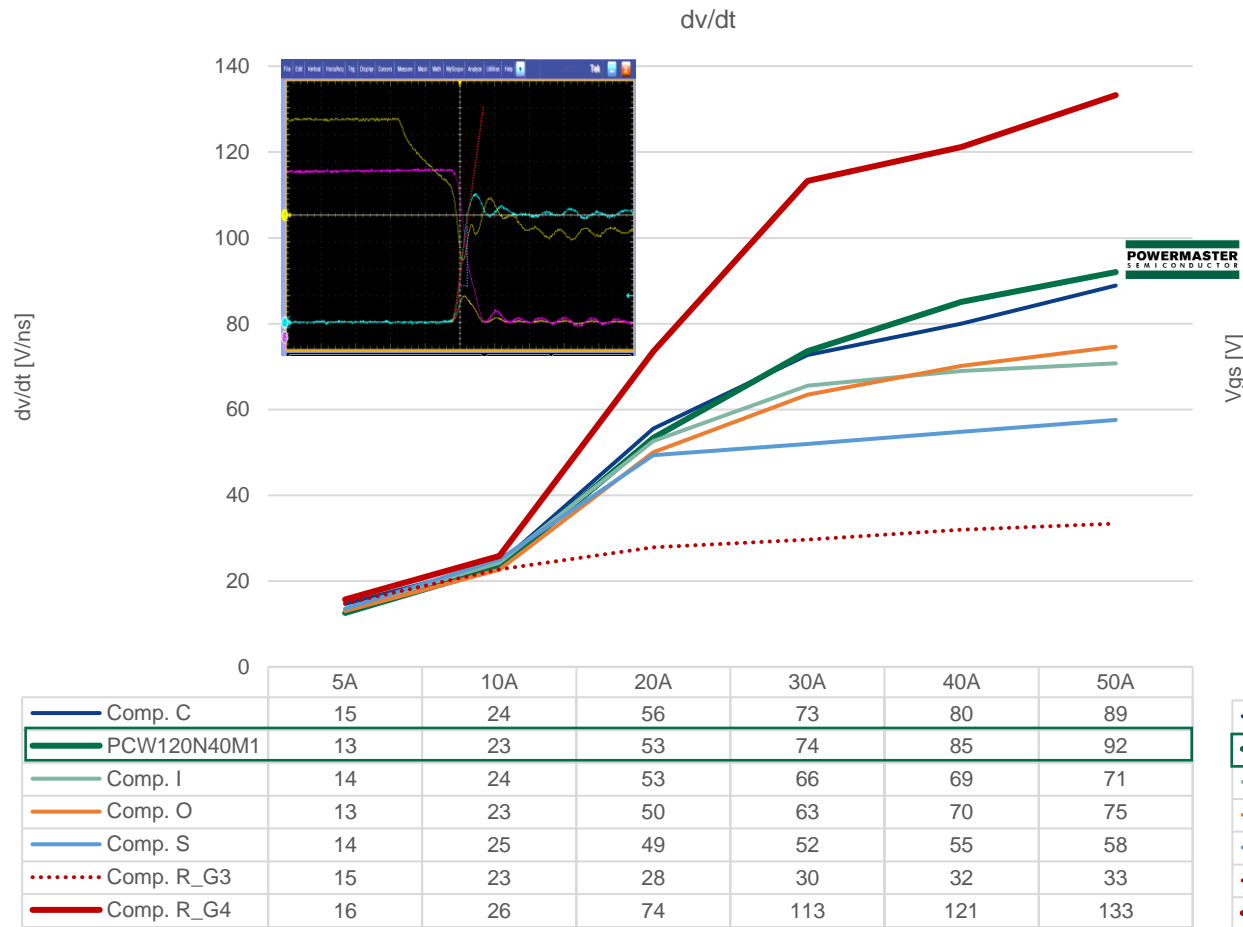


- Note
- * $V_{DD}=800V$, $R_G=2\Omega$, $V_{GS}=-3V\sim 18V$, $I_D=10A, 20A$, FWD=PCH120S10D1(1200V/10A)

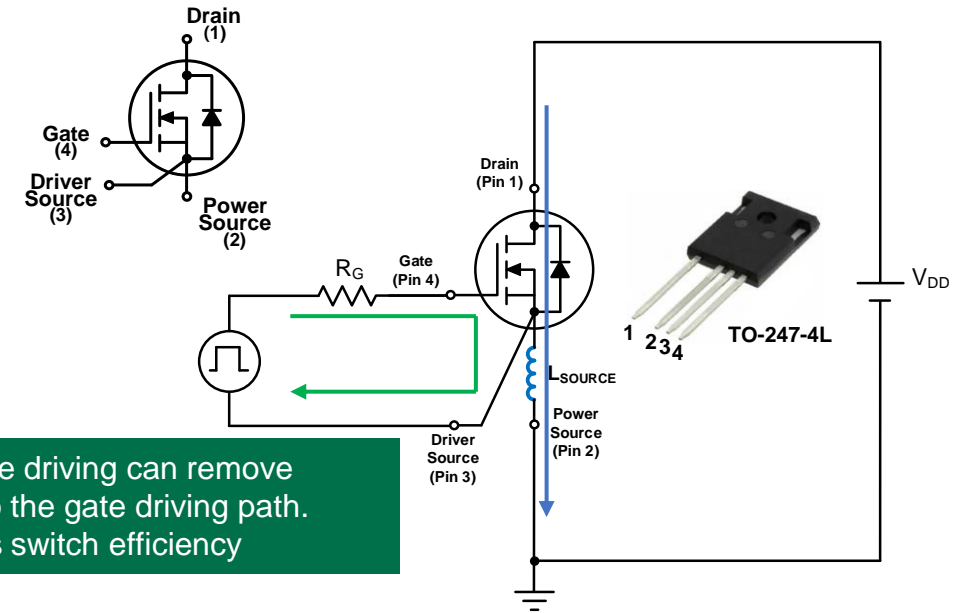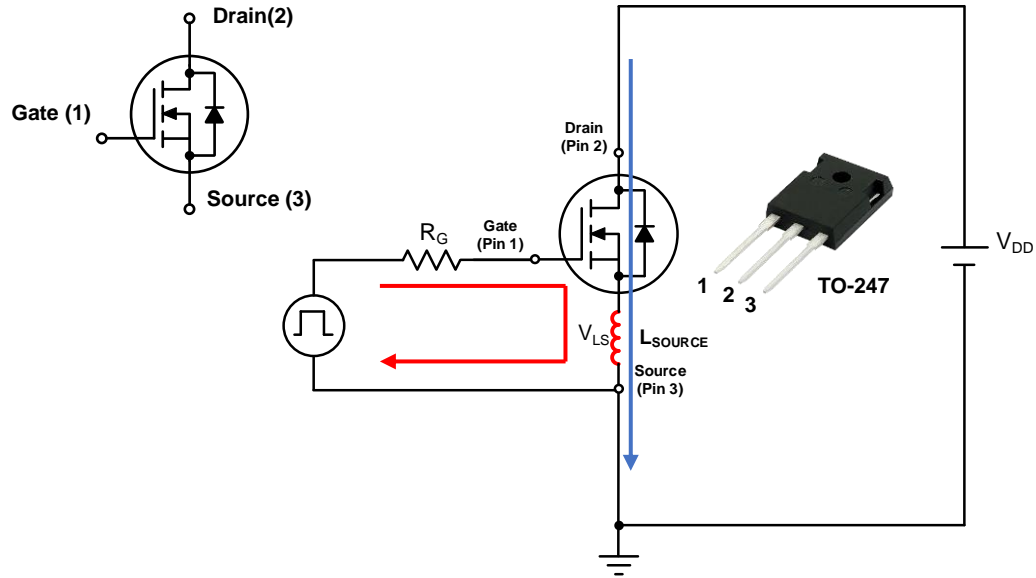TO-247-4L Kelvin Source Package' Benefits



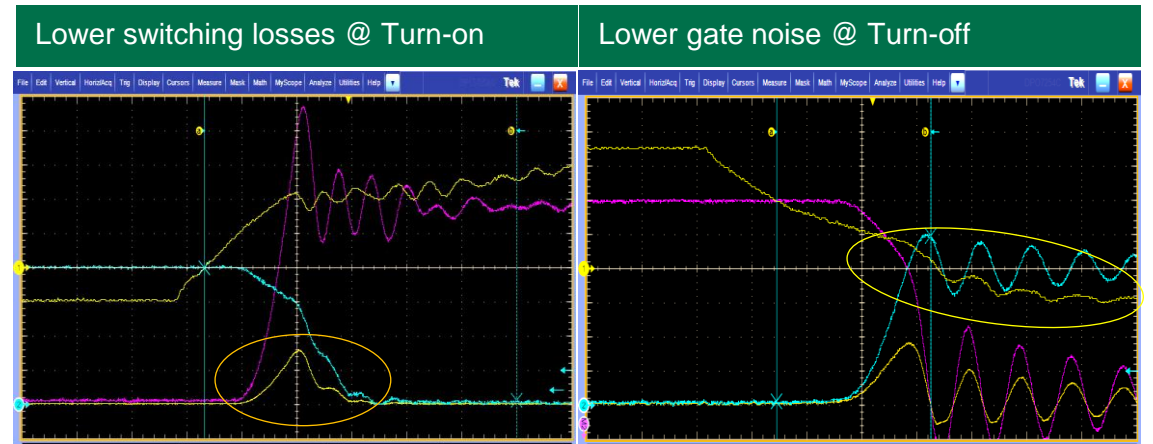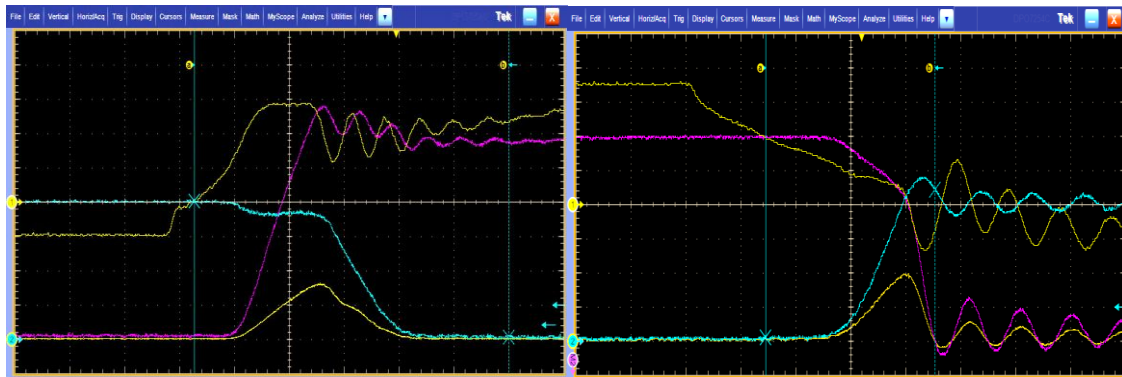
Kelvin source driving can remove L_{SOURCE} into the gate driving path.
 → Increases switch efficiency




Reduced Switching Loss by TO-247-4L Package

Switching Losses can be significantly improved !!

Turn-on Loss

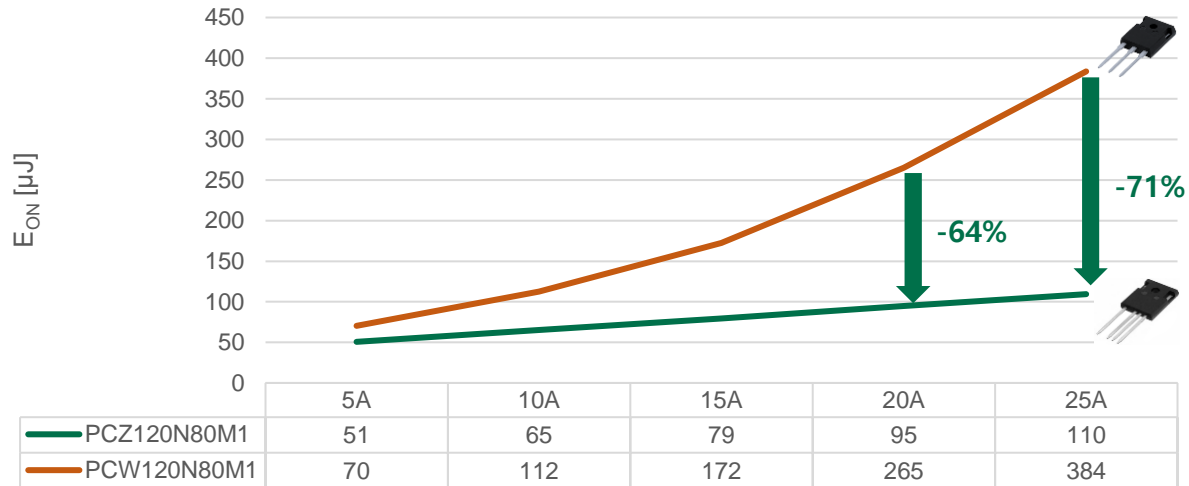

Turn-off Loss

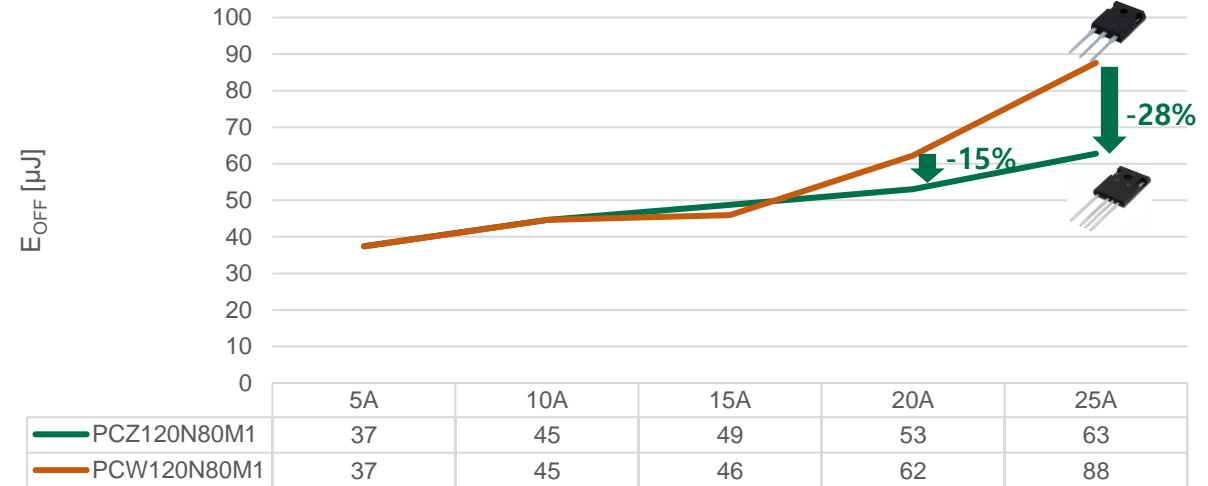

Color : TO-247 3L White : TO-247 4L


TO-247 4L Benefits

Turn-on

Turn-off

1200V / 80mΩ *e*SiC MOSFET Benchmark


PCZ120N80M1 vs. Competitors

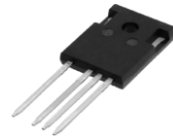


	PCZ120N80M1	Comp. I	Comp. O	Comp. R
BV_{DSS} [V]	1200	1200	1200	1200
I_D [A]	30	26	29	31
V_{GS_op} [V]	-5 / +18	0 / +18	-5 / +20	0 / +18
V_{GS_max} [V]	-10 / +22	-7 / +23	-15 / +25	-4 / +22
I_{GSS} [nA]	±100 ● (-10V / 22V)	±100 ● (-7V / 23V)	±1000 ● (-15V / 25V)	±100 ● (-4V / 22V)
$R_{DS(on)}$ [mΩ] (typ) / (max)	80 / 104	90 / 125	80 / 110	80 / 104
V_{TH} [V]	2.0 / 3.0 / 4.5	3.5 / 4.5 / 5.7	1.8 / 2.75 / 4.3	2.7 / - / 5.6
Int. R_G [Ω]	4.0	9.0	1.7	12.0
V_{SD} [V]	4.1	4.1	3.7	3.2
Q_G [nC]	52 ●	21 ●	56 ●	60 ●
E_{ON} [μJ] @ $I_D=20A$, $R_G=2Ω$	95 ●	88 ●	129 ●	168 ●
E_{OFF} [μJ] @ $I_D=20A$, $R_G=2Ω$	53 ●	40 ●	60 ●	117 ●

1200V / 80mΩ *e*SiC MOSFET Switching Losses

PCZ120N80M1 vs. Competitors

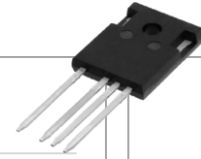


Turn-on Loss

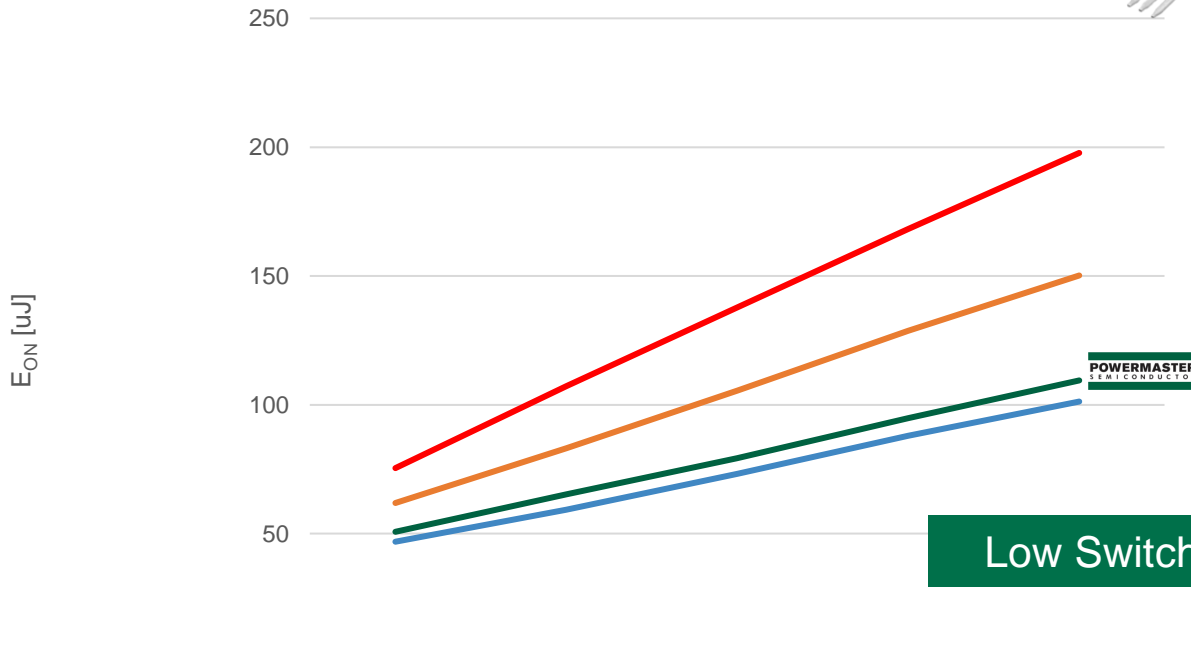

Low Switching Losses

	5A	10A	15A	20A	25A
PCZ120N80M1	51	65	79	95	110
Comp. I	47	59	73	88	101
Comp. O	62	83	106	129	150
Comp. R	75	107	138	168	198

Turn-off Loss

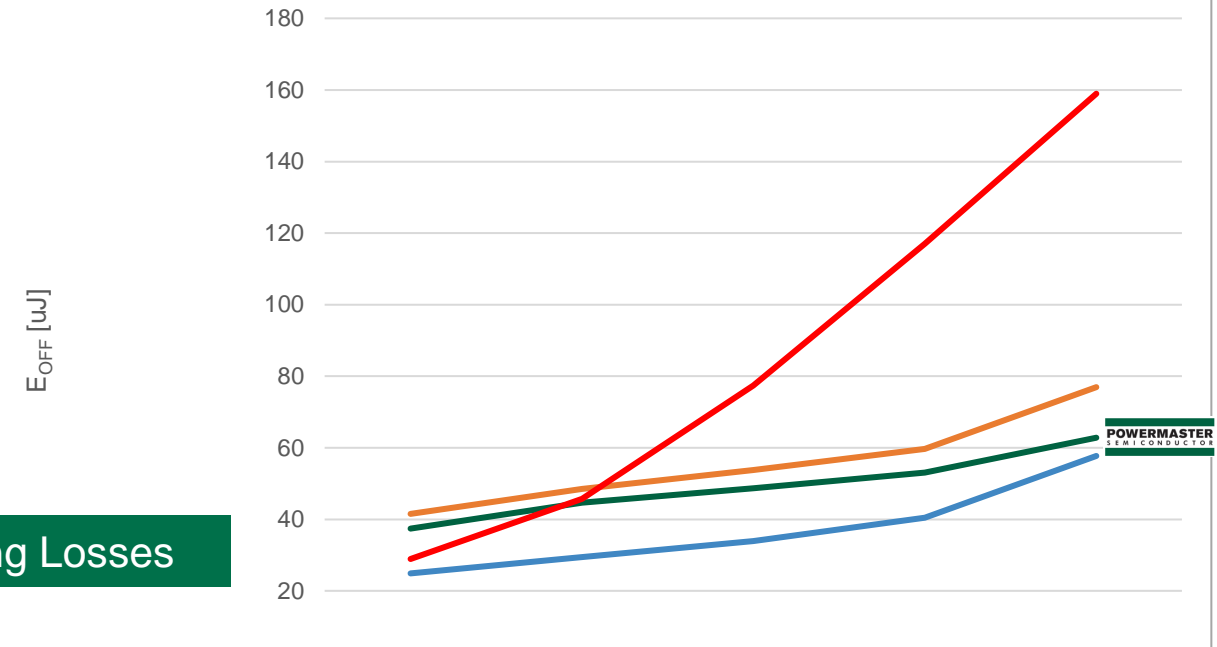

	5A	10A	15A	20A	25A
PCZ120N80M1	37	45	49	53	63
Comp. I	25	29	34	40	58
Comp. O	42	49	54	60	77
Comp. R	29	46	77	117	159


* Test condition : $V_{DD}=800V$, $V_{GS}=-3V/+18V$, FWD=PCH120S10D1, $R_G=2\Omega$

1200V / 80mΩ *e*SiC MOSFET Switching Performance

PCZ120N80M1 vs. Competitors


Turn-on

Turn-off

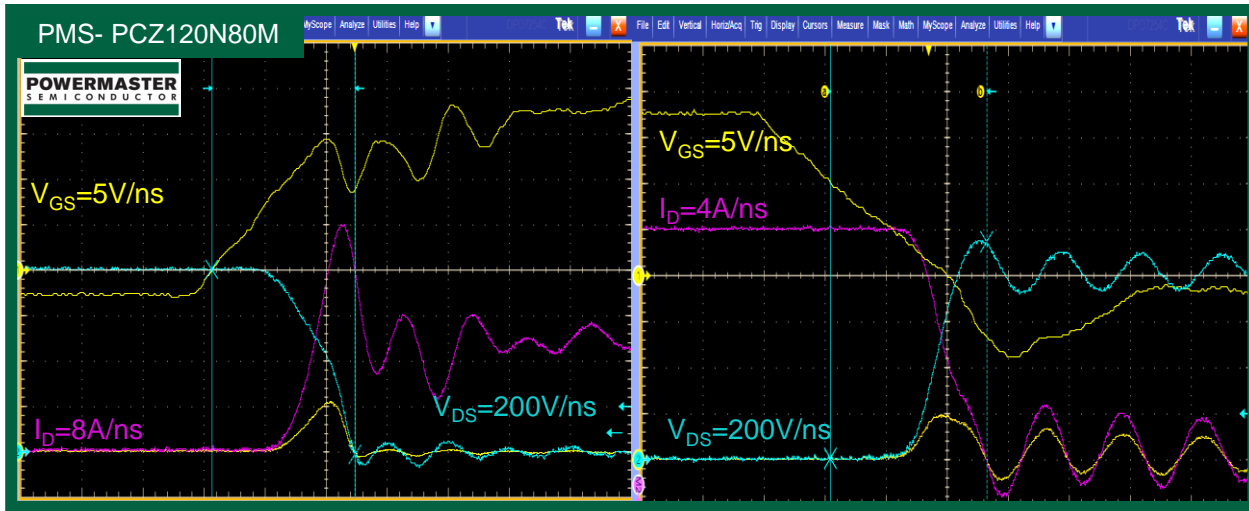


Turn-on

Turn-off

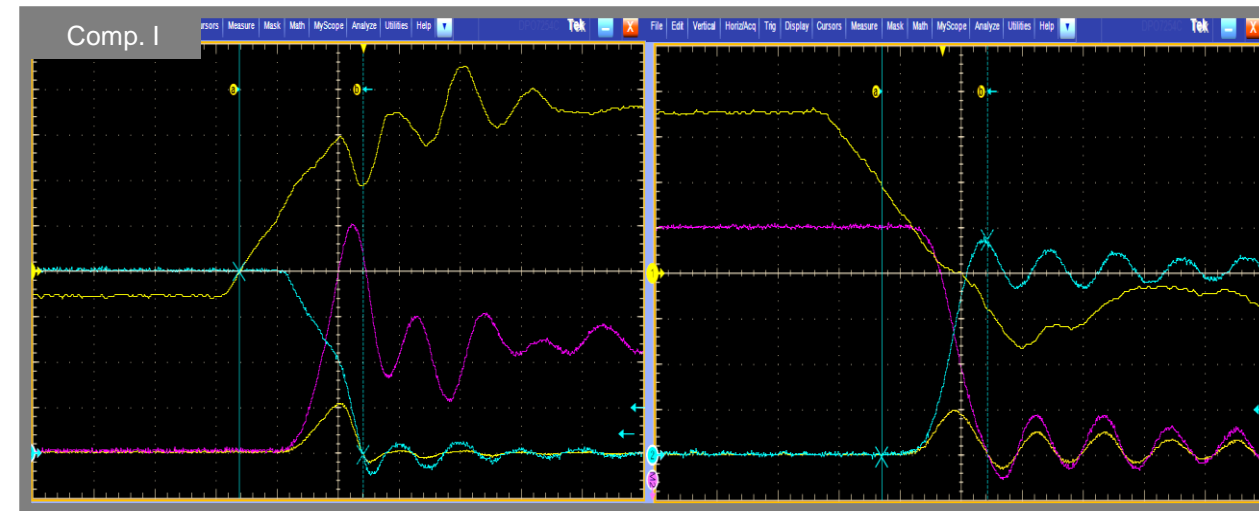


Turn-on

Turn-off

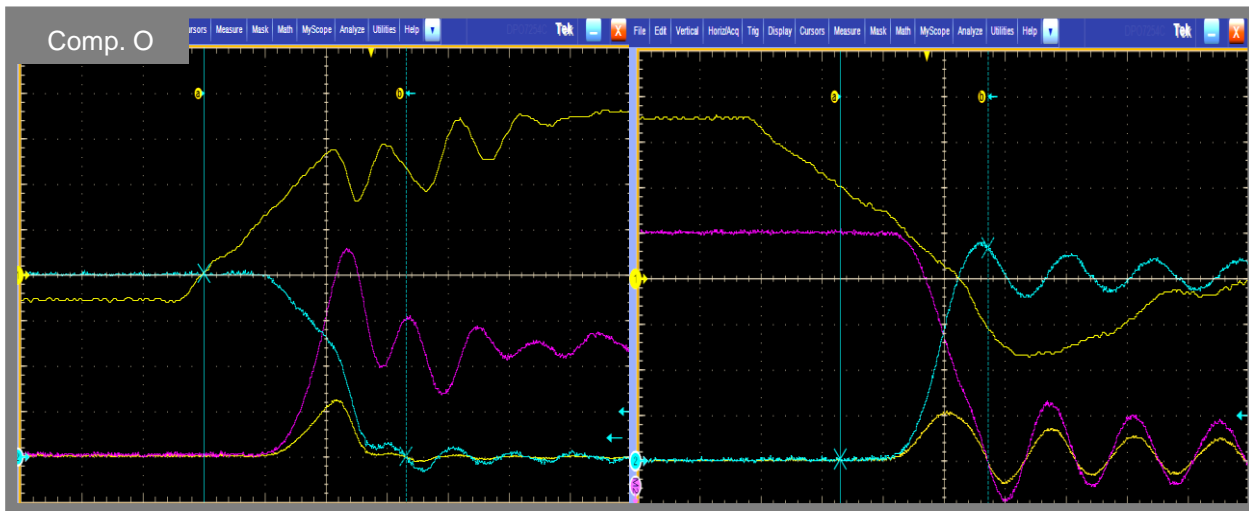

Turn-on

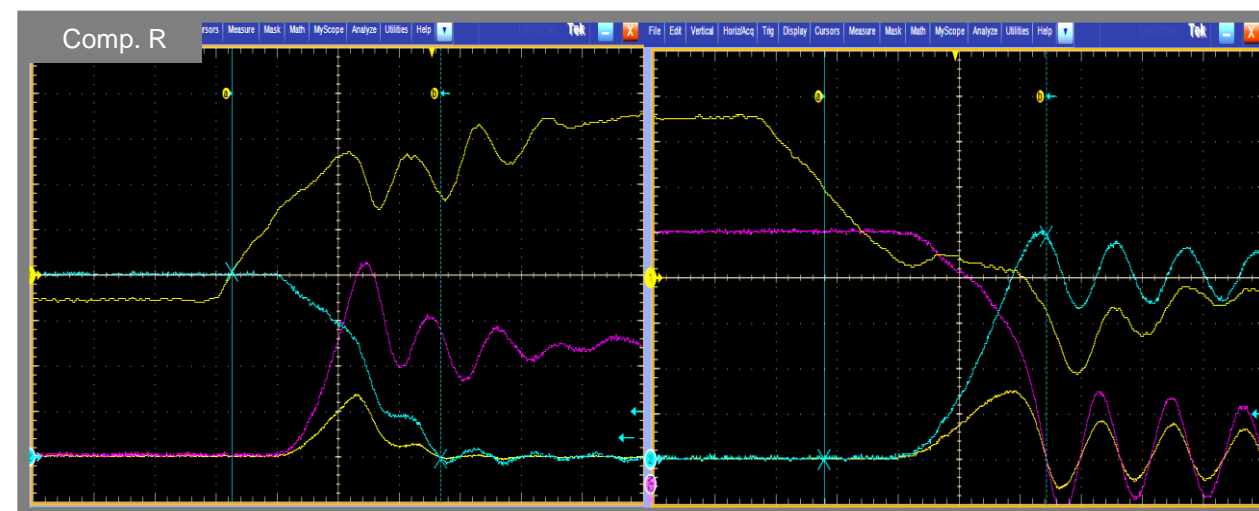


Turn-off



650V / 1200V *e*SiC MOSFET Portfolio

650V *e*SiC MOSFET Lineup




Solar | Server / Telecom | UPS | EV Charger | xEV(OBC)

R _{DS(ON)_typ} / PKG	Die	D2PAK 7L	TO-247 3L	TO-247 4L
				
18mΩ	*PCO65N18M1	*PCBF65N18M1(-A)	*PCW65N18M1(-A)	*PCZ65N18M1(-A)
27mΩ	*PCO65N27M1	*PCBF65N27M1(-A)	*PCW65N27M1(-A)	*PCZ65N27M1(-A)
48mΩ	*PCO65N48M1	*PCBF65N48M1(-A)	*PCW65N48M1(-A)	*PCZ65N48M1(-A)
72mΩ	*PCO65N72M1	*PCBF65N72M1(-A)	*PCW65N72M1(-A)	*PCZ65N72M1(-A)
107mΩ	*PCO65N107M1	*PCBF65N107M1(-A)	*PCW65N107M1(-A)	*PCZ65N107M1(-A)

* Coming soon (-A : Automotive Grade)

1200V *e*SiC MOSFET Lineup


Solar | UPS | EV Charger | xEV(OBC)

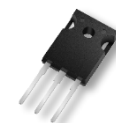R _{DS(ON)_typ} / PKG	Die	D2PAK 7L	TO-247 3L	TO-247 4L
				
21mΩ	PCO120N21M1	*PCBF120N21M1(-A)	PCW120N21M1(-A)	PCZ120N21M1(-A)
30mΩ	*PCO120N30M1	*PCBF120N30M1(-A)	*PCW120N30M1(-A)	*PCZ120N30M1(-A)
40mΩ	PCO120N40M1	*PCBF120N40M1(-A)	PCW120N40M1(-A)	PCZ120N40M1(-A)
60mΩ	*PCO120N60M1	*PCBF120N60M1(-A)	*PCW120N60M1(-A)	*PCZ120N60M1(-A)
80mΩ	PCO120N80M1	*PCBF120N80M1(-A)	PCW120N80M1(-A)	PCZ120N80M1(-A)

* Coming soon (-A : Automotive Grade)

eSiC MOSFET – Nomenclature

P C P 120 N 60 M1 - A

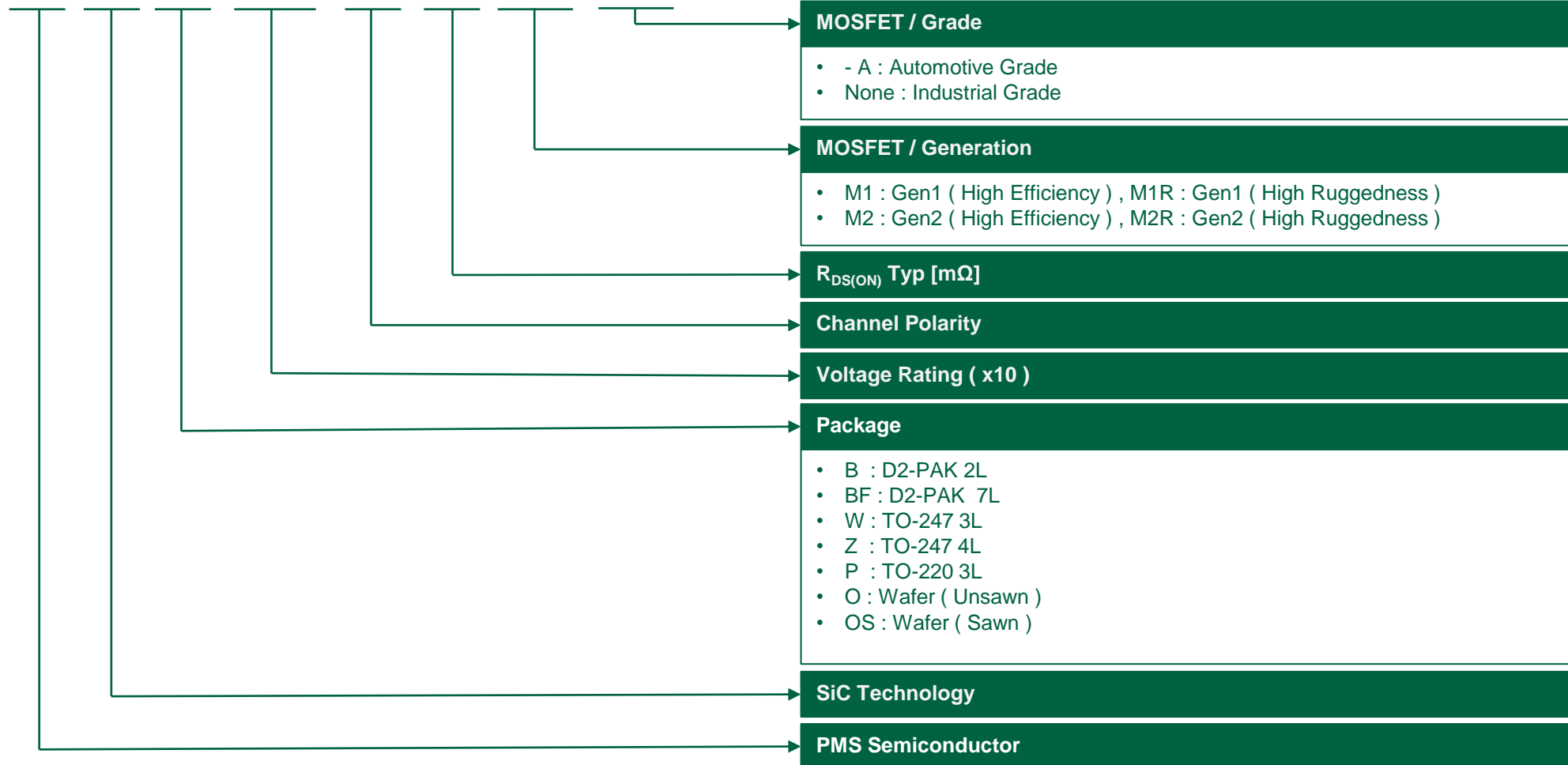

Important Notice

POWERMASTER
S E M I C O N D U C T O R

Masters of Power Solution

Experience Power Master's leading edge products and superb application engineers' design support at fair price

Important Notice

This document is only for information purpose and any information given herein shall in no event be regarded as a warranty, guarantee or description of any functionality, conditions and quality of PMS's products.

- Please refer to technical specification of product datasheet that provided by Power Master Semiconductor
- This document and any information herein may not be reproduced without prior written permission from Power Master Semiconductor
- This document is subject to change without notice.
- The products described herein and this document are subject to specific disclaimers
- Though Power Master Semiconductor works continually to improve quality and reliability. Customers are responsible for complying with safety standards and for providing adequate designs and safeguards for their systems.
- Customers are solely responsible for all aspects of their own design or applications, including but not limited to determining the appropriateness of the use of this product, determining the applicability of any information contained in this document.

Power Master Semiconductor – All rights reserved

