
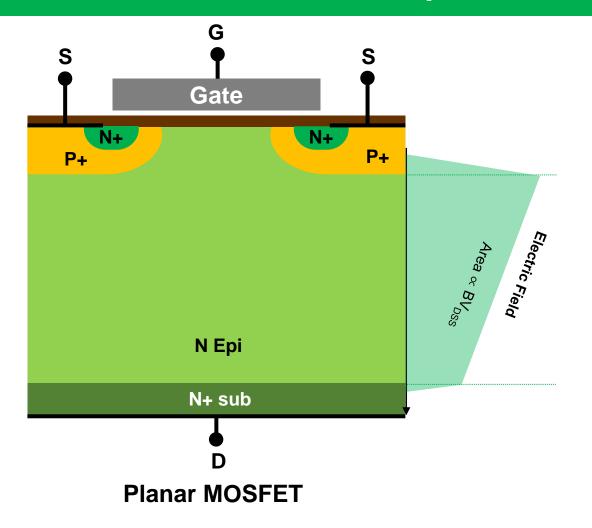


eMOS SJ MOSFET Selection Guide 2022

Advanced Power Master Semiconductor's Super-Junction MOSFET Technology

eMOS - Super Junction MOSFET Technology

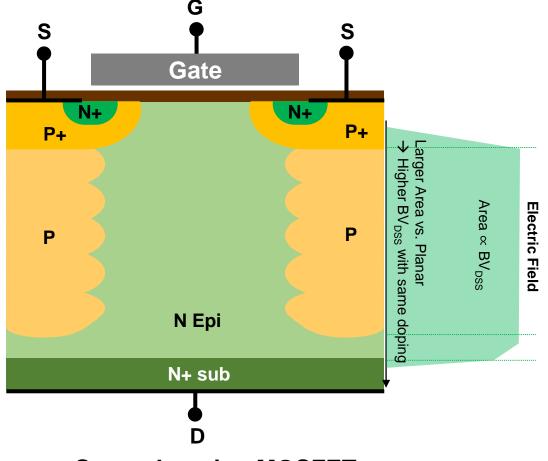




Super Junction MOSFET

- A linear relation between R_{DS(ON)} and BV_{DSS}
- Lower R_{DS(ON)} in same die size
- Smaller die size in same R_{DS(ON)}
- Low capacitance → Lower switching losses

eMOS for High and Low Power Applications

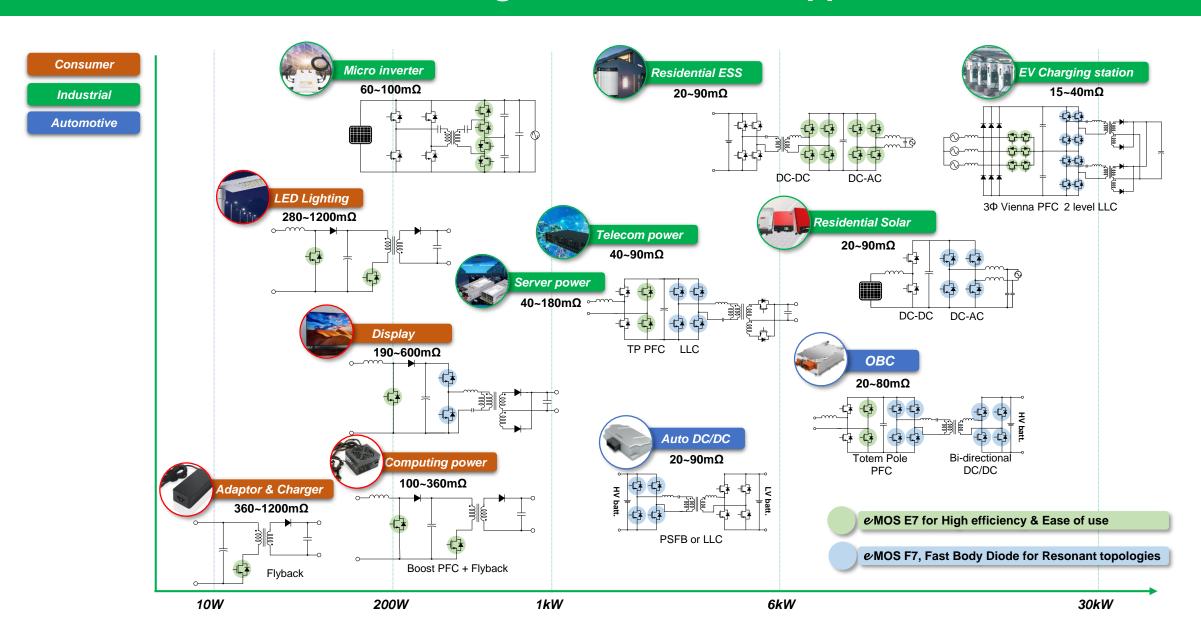

eMOS 7 Series - Features and Benefits

The eMOS 7 series is designed to target the world-class performance in the various applications ranging from low power to high power.

The MOS 7 series enables to offer high performance, cost-effective, and robust solution for AC/DC and DC/DC applications such as hard & soft switching with a wide range of package options.

The <a>MOS E7 is well-balanced combining <a>ease of use with an excellent efficiency performance and a reasonable price.

Key Features

- Excellent ruggedness
- Good switching behavior for hard and soft switching.
- Significant reduction of switching and conduction losses

Key Benefits

- Suitable for hard and soft switching (PFC and LLC)
- Ease of use and fast design-in through low ringing tendency and usage across PFC and PWM stages
- Simplified thermal management due to low switching and conduction losses
- Suitable for a wide variety of applications and power ranges

The **MOS** F7 is well-optimized for resonant topologies with an **excellent integrated body diode** performance.

Key Features

- Excellent body diode performance Smaller Q_{RR}
- Improved body diode dv/dt and di/dt ruggedness
- Lower E_{DYN}

Key Benefits

- Suitable for soft switching (LLC)
- Highest reliability for resonant topologies
- High light load efficiency.
- Suitable for a wide variety of applications and power ranges

eMOS E7 & F7 - Target Topologies

PFC (Hard Switching)



LLC / ZVS (DC-DC) (Soft Switching)




- High performance of body diode
- Smaller Q_{RR} for lower spikes
- Robust body diode for system reliability
- Reduced E_{DYN}
- Typ. V_{TH}=4V



ℳOS F7 by controlling carrier life-time

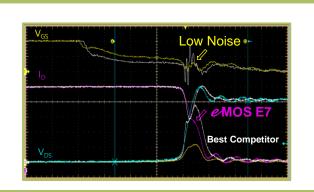- Balanced performance between efficiency & easy of use
- Low EMI noise, optimized gate & drain ringing
- Rugged body diode
- Optimized Capacitances
- Typ. V_{TH}=3.5V




eMOS E7 by optimizing charge balance of pillar

600V / 650V eMOS E7 Portfolio

eMOS E	7 (Easy Drive C Topologies	Adaptor	ATX Power Class Aud	s-D TV / LED	Server / Telecom UPS	EV Charger EV(OBC)
PKG	Die	DPAK	PQFN88	TO-220	TO-220F	TO-247 3L
R _{DS(ON)_max}						
28mΩ						PMW60N028E7
40mΩ						PMW60N040E7
70mΩ						PMW60N070E7
99mΩ			*PML60N0105E7	PMP60N099E7	PMF60N099E7	PMW60N099E7
120mΩ						
180mΩ	PMO60N180E7			PMP60N180E7	PMF60N180E7	
280mΩ	PMO60N280E7	PMD60N280E7		PMP60N280E7	PMF60N280E7	
380mΩ	PMO60N380E7	PMD60N380E7		PMP60N380E7	PMF60N380E7	
600mΩ	PMO60N600E7	PMD60N600E7			PMF60N600E7	
180mΩ	*PMO65N180E7					
280mΩ	*PMO65N280E7					
380mΩ	*PMO65N380E7					
600mΩ	*PMO65N600E7					
1200mΩ	*PMO65N1200E7					

600V / 650V eMOS F7 Portfolio

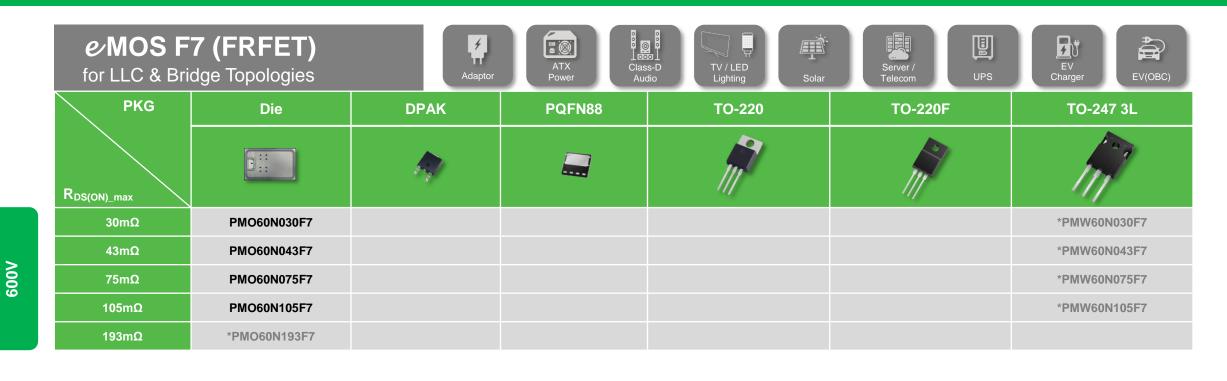


|--|

43mΩ	*PMO65N043F7			*PMW65N043F7
310mΩ	*PMO65N310F7		*PMF65N310F7	

^{*} Coming soon

eMOS - Nomenclature

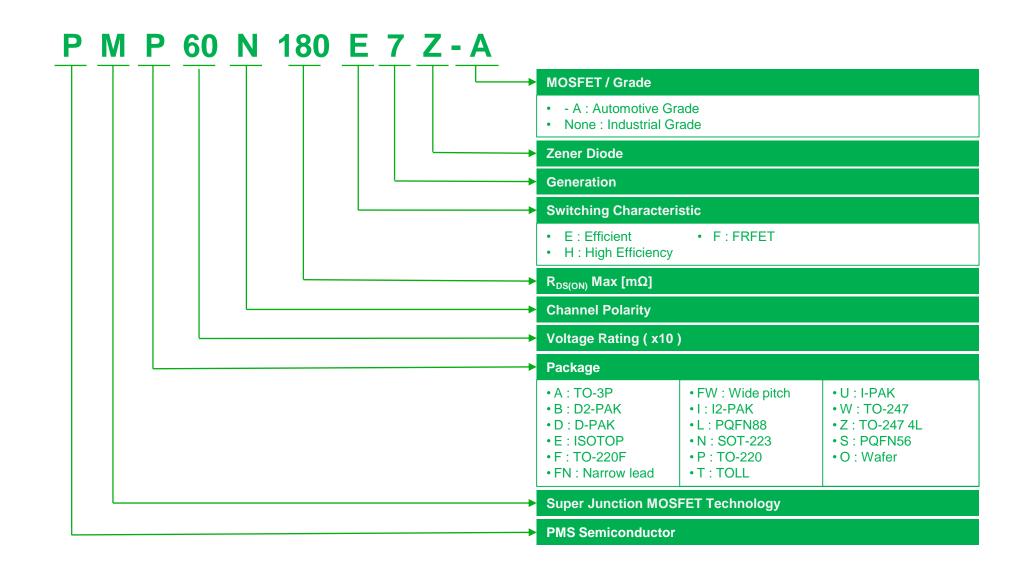

Important Notice

POWERMASTER SEMICONDUCTOR

Masters of Power Solution

Experience Power Master's leading edge products and superb application engineers' design support at fair price

Important Notice

This document is only for information purpose and any information given herein shall in no event be regarded as a warranty, guarantee or description of any functionality, conditions and quality of PMS's products.

- Please refer to technical specification of product datasheet that provided by Power Master Semiconductor
- This document and any information herein may not be reproduced without prior written permission from Power Master Semiconductor
- This document is subject to change without notice.
- · The products described herein and this document are subject to specific disclaimers
- Though Power Master Semiconductor works continually to improve quality and reliability. Customers are responsible for complying with safety standards and for providing adequate designs and safeguards for their systems.
- Customers are solely responsible for all aspects of their own design or applications, including but not limited to determining the appropriateness of the use of this product, determining the applicability of any information contained in this document

Power Master Semiconductor - All rights reserved

